This design shows the LED in the flower.

Positive LED leg   Negative LED leg

Use a BRIGHT color to represent your positive line

Use a DARK color to represent your negative line
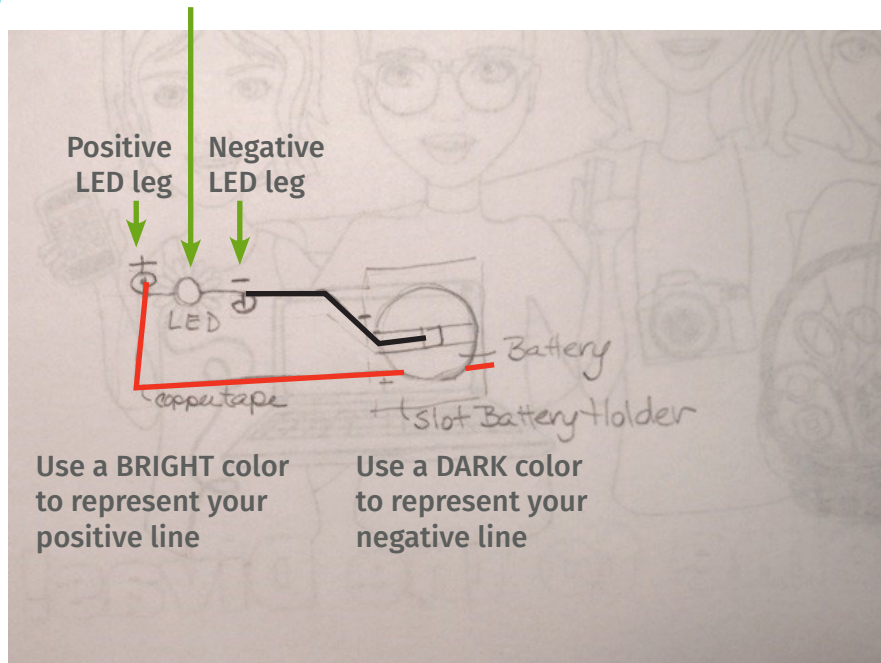
Circuit design completed.
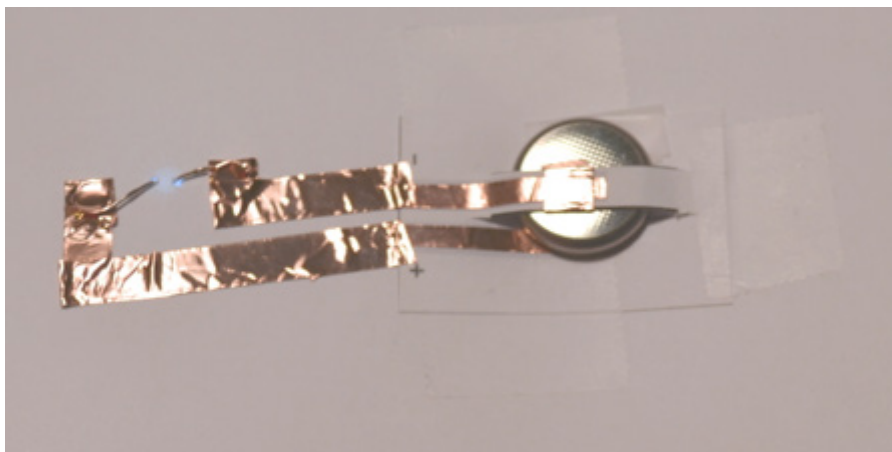
Now draw your circuit design!